

Attendance

Computer Organisation

Topic 4

Digital Logic (Part 2)

Outline

- Sequential Circuits
 - Flip-Flops
 - Registers
 - Counters
- Programmable Logic Devices
 - Programmable Logic Array
 - Field-Programmable Gate Array

Introduction

- Combinational circuits
 - Implement **functions** of a computer
 - Outputs depend entirely on the present input
 - **No memory** (except for ROM)

Introduction

- **Storage** elements
 - Devices that are capable of storing binary information (which defines the state of the sequential circuit)

Sequential Circuit

- Current output depends on the current input and the current state of the circuit
- Consists of a combinational circuit to which storage elements are connected to form a **feedback path**


Flip-Flops

- **Simplest** sequential circuit
- It has the capability to **"store"** **information** (1-bit memory)

Flip-Flops

- A **bistable** device
 - Exists in one of two states
 - In the absence of the input remains in that state
- With **two outputs**, Q & $\overline{Q}$, which are the complement of each other


Flip-Flops

 

S-R Latch

- 2 inputs
 - S (Set) and R (Reset)
- 2 outputs
 - Q and $\bar{Q}$
- 2 NOR gates connected in a feedback manner


Reset = 0

 

Set = 1

S-R Latch

 
- $S = 0, R = 0, Q = 0$
 - Inputs to lower NOR gate are $Q = 0, S = 0$



Flip-flops remains stable in this state

S-R Latch

 - $S = 0, R = 0, Q = 1$
 - Inputs to lower NOR gate are $Q = 1, S = 0$



Flip-flops remains stable in this state

Setting the S-R Latch


S-R Latch

Let's say initially

- $S=0, R=0, Q=0, \bar{Q}=1$

Then $S=1$

 
- ✓ Inputs to lower NOR gate are $S=1, Q=0$
- ✓ After Δt , output of lower NOR gate will be $\bar{Q}=0$
- ✓ Inputs to the upper NOR gate become $R=0, \bar{Q}=0$
- ✓ After another Δt , output $Q=1$



S-R Latch

After that, if $S=0$

 - Inputs to lower NOR gate are $S=0$, $Q=1$
- After Δt , output of lower NOR gate will be $Q=0$
- Inputs to the upper NOR gate become $R=0$, $Q=0$
- After another Δt , output $Q=1$



Reset the S-R Latch

S-R Latch


Initially $S=0$, $R=0$, $Q=1$, $\bar{Q}=0$

$R=1$

- Inputs to upper NOR gate are $R=1$, $Q=0$
- After Δt , output of upper NOR gate will be $Q=0$
- Inputs to the lower NOR gate become $S=0$, $Q=0$
- After another Δt , output $\bar{Q}=1$


• After that, if $R=0$

- $Q=0$, $\bar{Q}=1$

 

S-R Latch

NOR S-R Latch Timing Diagram

 

S-R Latch

- Summary
 - S writes a 1 to Q
 - R writes a 0 to Q
 - S=1 and R=1 at the same time are not allowed
 - Inconsistent output

(a) Characteristic Table		
Current Inputs	Current State	Next State
SR	Q_n	Q_{n+1}
00	0	0
00	1	1
01	0	0
01	1	0
10	0	1
10	1	1
11	0	—
11	1	—

(b) Simplified Characteristic Table		
S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	—

S-R Latch

(c) Response to Series of Inputs


t	0	1	2	3	4	5	6	7	8	9
S	1	0	0	0	0	0	0	0	1	0
R	0	0	0	1	0	0	1	0	0	0
Q_{n+1}	1	1	1	0	0	0	0	0	1	1

Clocked S-R Flip-Flop

- S-R latch
 - Output changes in **response** to a change in input
 - Brief time **delay**
 - **Asynchronous**


Clocked S-R Flip-Flop

 - Events in digital computer are **synchronised** according to clock pulse
 - Clocked S-R flip-flop



D Flip-Flop

 - A single input ensures that **$S=R=1$ never occurs**
 - Inverter ensures (non-clock) inputs to the AND gates are opposite
- Also called **data** flip-flop



D	Q_{n+1}
0	0
1	1

Reset


Set

J-K Flip-Flop

- Similar to S-R flip-flop
- **All combinations** of input values are **valid**


J-K Flip-Flop

 - When $J=K=1$ it acts as a **toggle** function, the output is a **reverse** of the present state






J-K Flip-Flop

 - When $J=K=1$ it acts as a **toggle** function, the output is a **reverse** of the present state



S-R vs. J-K vs. D Flip-Flops

   Name	Graphical Symbol	Truth Table															
S-R		<table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>-</td></tr></table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	-
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	-															
J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

S = to set

R = to reset

S = R = 1, not ALLOWED

J = to set

K = to reset

S = R = 1, it will toggle the Q value

Input value will be channelled to output

Outline


- Sequential Circuits
 - Flip-Flops
 - Registers
 - Counters
- Programmable Logic Devices
 - Programmable Logic Array
 - Field-Programmable Gate Array

Registers

- Digital circuit within CPU to **store** one or more bits of data
- Two types:
 - **Parallel** registers
 - **Shift** registers


Parallel Registers

 - Supports **simultaneous** reading or writing to a set of 1-bit memories
- Uses **D** flip-flops



Shift Registers

 - Accepts/**transfers** information **serially**
 - Use (clocked) D flip-flops (or even S-R)
 - Input only to left-most flip-flop
 - Data are shifted one position at every clock pulse
 - Use to interface to serial I/O devices, perform logical shift/rotate functions (ALU), etc.



Counters


- Register which increment its value by modulo of its capacity
- n flip-flop has the capacity up to $2^n - 1$
 - Beyond maximum, is set to 0
- E.g. CPU's program counter

4 flip flops = $2^4 - 1 = 15$ counters

Ripple Counter

- **Slow**

 
- Output of one flip-flop **triggers a change in the next** flip-flop (ripple effect)
- The counter is incremented at each clock pulse (0000, 0001, 0010, 0011, ... 1111, 0000)




Ripple Counter

- **J and K inputs** to each flip-flop are **held at 1**
 - When there is clock pulse, output Q is **inverted** (0 to 1, 1 to 0)
- Q_0 is least significant bit

Ripple Counter

 


Will be
toggling
most often

 

When Q₀
becomes 0,
then only Q₁
becomes 1

Ripple Counter

 

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Q0 toggle the most often

Synchronous Counter

- **Faster**
 - All flip-flops **change state at the same time**
 - CPUs use synchronous counters
- E.g. 3-bit counter using J-K flip-flop
 - 3 flip-flops (A, B, and C – A is least significant bit)
 - Construct truth table

Synchronous Counter

C	B	A	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	0	d	0	d	1	d
0	0	1	0	d	1	d	d	1
0	1	0	0	d	d	0	1	d
0	1	1	1	d	d	1	d	1
1	0	0	d	0	0	d	1	d
1	0	1	d	0	1	d	d	1
1	1	0	d	0	d	0	1	d
1	1	1	d	1	d	1	d	1

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q}_{n+1}$

Q_n	J	K	Q_{n+1}
0	0	d	0
0	1	d	1
1	d	1	0
1	d	0	1

Synchronous Counter

MSB

LSB

S R

C	B	A	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	0	d	0	d	1	d
0	0	1	0	d	1	d	d	1
0	1	0	0	d	d	0	1	d
0	1	1	1	d	d	1	d	1
1	0	0	d	0	0	d	1	d
1	0	1	d	0	1	d	d	1
1	1	0	d	0	d	0	1	d
1	1	1	d	1	d	1	d	1

Set & Toggle

Toggle & Reset

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

Q_n	J	K	Q_{n+1}
0	0	d	0
0	1	d	1
1	d	1	0
1	d	0	1

Synchronous Counter

$J_c = BA$

		BA			
		00	01	11	10
C	0			1	
	1	d	d	d	d

$K_c = BA$

		BA			
		00	01	11	10
C	0	d	d	d	d
	1			1	

$J_b = A$

		BA			
		00	01	11	10
C	0		1	d	d
	1		1	d	d

$K_b = A$

		BA			
		00	01	11	10
C	0	d	d	1	
	1	d	d	1	

$J_a = 1$

		BA			
		00	01	11	10
C	0	1	d	d	1
	1	1	d	d	1


$K_a = 1$

		BA			
		00	01	11	10
C	0	d	1	1	d
	1	d	1	1	d

C	B	A	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	0	d	0	d	1	d
0	0	1	0	d	1	d	d	1
0	1	0	0	d	d	0	1	d
0	1	1	1	d	d	1	d	1
1	0	0	d	0	0	d	1	d
1	0	1	d	0	1	d	d	1
1	1	0	d	0	d	0	1	d
1	1	1	d	1	d	1	d	1

Synchronous Counter

 - $J_a = 1$
- $K_a = 1$
- $J_b = A$
- $K_b = A$
- $J_c = BA$
- $K_c = BA$



Outline



- Sequential Circuits
 - Flip-Flops
 - Registers
 - Counters
- Programmable Logic Devices
 - Programmable Logic Array
 - Field-Programmable Gate Array

Programmable Logic Devices

- So far, individual **gates are building blocks**
 - Any function can be realised

Programmable Logic Devices

  - Early integrated circuits using SSI provided 1 to 10 gates on a chip
 - To construct a logic function, a **number of these chips are laid out** and the appropriate pin interconnections are made



Programmable Logic Devices

- Increasing levels of integration made it possible to put **more gates on a chip** and to make gate interconnections on the chip as well.
- Advantages:
 - Decreased cost and size
 - Increased speed

Programmable Logic Devices


- However,
 - For each logic function, layout of gates and **interconnections must be designed**
 - **Cost and time** involved for **custom chips** design is high

Programmable Logic Devices

- Thus,
- it becomes attractive to develop a **general-purpose chip** that can be readily adapted to specific purposes
- This is the intent of the programmable logic device (PLD)


Programmable Logic Devices

 - Programmable Logic Array (PLA)
 - A relatively small PLD that contains **two levels** of logic, an **AND-plane** and an **OR-plane**, where **both levels are programmable**



Programmable Logic Devices

 - Programmable Array Logic (PAL)
 - A relatively small PLD that has a **programmable AND-plane** followed by a **fixed OR-plane**



Programmable Logic Devices

- **Simple** PLD (SPLD)
 - A PLA or PAL
- **Complex** PLD (CPLD)
 - A more complex PLD that consists of an arrangement of multiple SPLD-like blocks on a single chip


Programmable Logic Devices

- **Field-Programmable Gate Array (FPGA)**
 - A general structure that allows very high logic capacity
 - Whereas CPLDs feature logic resources with a wide number of inputs (AND planes), FPGAs offer more narrow logic resources
 - FPGAs also offer a higher ratio of flip-flops to logic resources than do CPLDs
- **Logic Block**
 - A relatively small circuit block that is replicated in an array in an FPD

Programmable Logic Array

- Based on fact that any Boolean function can be **expressed in SOP**
- Consists of NOT, AND, and OR gates
- Each chip input is NOTed
- Output of each AND gate is available to each OR gate
- Output of each OR gate is a chip output
- Appropriate connects are made to implement a particular SOP expression


Programmable Logic Array

 

Programmable Logic Array

- PLAs manufactured in 2 ways
 - Every possible connection is made through a **fuse** at every intersection
 - Undesired connections are removed by blowing the fuses
 - Field Programmable Logic Array
 - Proper connections made during fabrication
- PLAs provide flexible, inexpensive way of implementing digital logic functions

Programmable Logic Array

 

Field-Programmable Gate Array

- PLA is an example of SPLD
- Problem is that the structure of programmable logic planes **grows too quickly in size** as number of inputs increased


Field-Programmable Gate Array

- Solution is to integrate **multiple SPLD onto single chip**
 - Provide interconnect to programmably connect the SPLD blocks together
 - Complex PLDs (CPLDs)
 - Most important type is FPGA

Field-Programmable Gate Array


- FPGA consists of an **array of uncommitted circuit elements**
- Key components
 - Logic block – computation takes place
 - I/O block – connects I/O pins to circuitry on chip
 - Interconnect – establish connections among I/O blocks and logic blocks

Field-Programmable Gate Array

 

Field-Programmable Gate Array

 - Logic block is either combinational or sequential circuit
 - Programming is done by downloading contents of truth table



Field-Programmable Gate Array



A person is sitting on a grassy bank next to a body of water. In the background, there are trees and a building. A bicycle is parked on the grass to the right of the person. The scene is captured in a low-angle shot, emphasizing the grass in the foreground.

Reflection...

From the lecture today,
I learnt...

Link on eLearn / Chat